

Code No: **R164202B**

R16

Set No. 1

IV B.Tech II Semester Advanced Supplementary Examinations, Aug/Sep - 2022
FLEXIBLE ALTERNATING CURRENT TRANSMISSION SYSTEMS

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70

Question paper consists of Part-A and Part-B

Answer ALL sub questions from Part-A

Answer any FOUR questions from Part-B

PART-A(14 Marks)

1. a) What are the basic types of FACTS controllers? [2]
b) How is Square wave voltage harmonics defined? [2]
c) What do you mean by power oscillation damping? [2]
d) Distinguish between thyristor-controlled reactor and thyristor switched capacitor [3]
e) List the objectives of Series compensation [3]
f) Draw the schematic diagram of UPFC [2]

PART-B(4x14 = 56 Marks)

2. a) Explain the various stability issues that limit the transmission capacity [7]
b) List and explain the requirements and characteristics of high power devices in FACTS devices [7]
3. a) Explain the operation of a three phase full wave voltage sourced converter with necessary supporting waveforms [7]
b) Compare current source converter with voltage source converter. [7]
4. a) Explain in detail about the Two – machine power system with an ideal midpoint reactive compensator with corresponding phasor diagram [7]
b) Describe the improvement of transient stability with shunt compensation. [7]
5. a) Explain the functional control scheme of the Fixed capacitor, Thyristor – controlled reactor type static VAR generator [7]
b) Write about summary of compensation control. [7]
6. a) Describe the concept of series capacitive compensation. [7]
b) Explain the operation of GTO – controlled series capacitor with relevant waveforms [7]
7. Write short notes on the following:
i)operation of Unified power flow controller [7]
ii)comparison of UPFC to controlled Series compensators [7]

