

Code No: **R1641022**

**R16**

**Set No. 1**

**IV B.Tech I Semester Regular/Supplementary Examinations, Jan/Feb - 2022**

**LINEAR IC APPLICATIONS**  
(Electrical and Electronics Engineering)

**Time: 3 hours**

**Max. Marks: 70**

*Question paper consists of Part-A and Part-B*

*Answer ALL sub questions from Part-A*

*Answer any FOUR questions from Part-B*

\*\*\*\*\*

**PART-A (14 Marks)**

1. a) What is meant by differential amplifier? [2]  
b) Define input offset current. [3]  
c) List the advantages of Voltage Follower. [2]  
d) Define frequency scaling. [2]  
e) List the applications of Monostable Multivibrator. [3]  
f) Write the expression for Accuracy. [2]

**PART-B (4x14 = 56 Marks)**

2. a) Write brief notes on level translator with necessary schematics. [7]  
b) Discuss the analysis of differential amplifier. [7]
3. a) Draw and explain the output stage of IC 741 op-amp. [7]  
b) What is the stability of an op-amp? Explain the various stability specifications. [7]
4. a) Mention some applications of an instrumentation amplifier. [7]  
b) Derive the output voltage  $V_0$  of an integrator circuit. [7]
5. a) Derive the expression for the transfer function of II order highpass filter. [7]  
b) Design a wide band reject filter having  $f_H = 200$  Hz and  $f_L = 1$  kHz. Assume suitable data. [7]
6. a) Derive the expression of time delay of a monostable multivibrator using 555 timer. [7]  
b) Draw the block schematic of 555 IC. [7]
7. a) With a neat circuit diagram, explain the functioning of an inverted R-2R ladder type digital to analog converter. [7]  
b) Calculate the conversion time for a full scale input in case of a 12-bit counter type analog to digital converter driven by 2 MHz clock. [7]

