

III B. Tech II Semester Supplementary Examinations, December -2023**ELECTRIC DRIVES**

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70

Answer any **FIVE** Questions **ONE** Question from **Each unit**

All Questions Carry Equal Marks

UNIT-I

1. a) List down the various components of load torques. [7M]
- b) Illustrate the four quadrant operation of drive considering hoist as an example. [7M]

(OR)

2. a) Explain briefly about steady state stability of motor load systems. [7M]
- b) Explain in detail about plugging and regenerative braking. [7M]

UNIT-II

3. Explain in detail about single phase half-controlled rectifier control of self excited motor in continuous and discontinuous conduction mode with waveforms. [14M]

(OR)

4. A 220V, 960 rpm, 12.8 A separately excited DC motor has armature circuit resistance and inductance of 2 ohm and 150 mH, respectively. It is fed from a single-phase fully-controlled rectifier with an ac source voltage of 230V, 50Hz. Calculate [14M]
 - (i) Motor torque for $\alpha = 60^\circ$ and Speed = 600 rpm
 - (ii) Motor speed for $\alpha = 60^\circ$ and $T = 20$ N-m.

UNIT-III

5. With the help of waveforms, explain in detail about two quadrant DC-DC converter fed separately excited DC motor, when operating in continuous mode? [14M]

(OR)

6. a) Discuss the operation of single quadrant DC-DC converter fed DC motor drive. [7M]
- b) Explain closed loop operation of self excited DC motor with neat diagram. [7M]

UNIT-IV

7. a) Explain variable frequency control of induction motor to obtain speeds below and above base speed. Derive the necessary equations. [7M]
- b) With neat waveforms and circuit diagram, explain the stator voltage control of three phase induction motor using three phase AC voltage regulator. [7M]

(OR)

8. a) Draw the circuit diagram and explain the operation of rotor-resistance control of induction motor. Mention the advantages and disadvantages of the above method of control. [7M]
- b) Explain closed loop operation of slip controlled PWM inverter fed induction motor drives. [7M]

UNIT-V

9. a) Describe separate control mode of operation of a synchronous motor drive in detail. [7M]
- b) Draw the block diagram of closed loop synchronous drive fed from VSI and explain its operation. [7M]

(OR)

1 of 2

|||||

10. A 5MW, 3 ϕ , 11kV, star-connected, 6-pole, 50 Hz, 0.9 leading pf [14M]
synchronous motor has $X_s = 10\Omega$ and $R_s = 0\Omega$. The rated field current is 50A.
Assume that stator resistance is to be neglected. The machine is controlled by
variable frequency control at constant V/f ratio up to base speed and constant
V above base speed. Determine
- The torque and the field current for the rated armature current of 750
rpm and 0.8 pf leading.
 - The armature current and pf for half the rated motor torque, 1500 rpm
and rated field current.

