

**III B. Tech II Semester Regular/Supplementary Examinations, August-2021****POWER SYSTEM ANALYSIS**

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70

Note: 1. Question Paper consists of two parts (Part-A and Part-B)

2. Answer ALL the question in Part-A

3. Answer any **FOUR** Questions from **Part-B**


~~~~~

**PART -A****(14 Marks)**


1. a) What is the need of single line diagram in power systems? [2M]
- b) Define slack bus. [2M]
- c) Mention different types of short circuit faults which may occur in power system. [2M]
- d) What is the importance of representing power system with its equivalent reactance diagram in short circuit studies? [3M]
- e) Write the order of severity of short circuit faults on power system. [3M]
- f) Define critical clearing angle. [2M]

**PART -B****(56 Marks)**

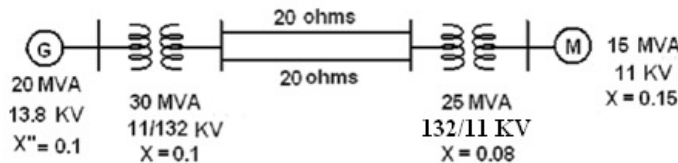2. a) Derive per unit impedance in terms of base MVA and base KV for a three phase system. [7M]
- b) Draw the P.U diagram for the circuit shown in below figure. Choose base values as relevant to the given quantities. [7M]




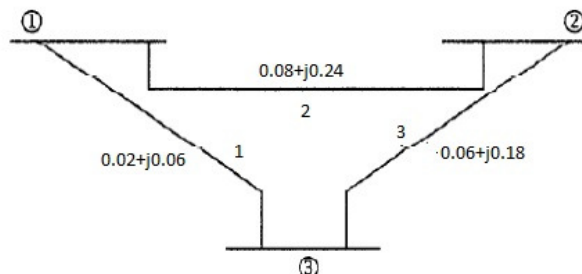3. a) Explain how the buses are classified in the calculation of power flow? [4M]
- b) Explain the step by step computational procedure for the Newton-Raphson method of load flow studies. [10M]
4. a) Form  $Z_{BUS}$  through step-by-step method of building algorithm for the power system network shown below. [7M]



- b) Explain in detail the procedure of addition of a branch or link to a partial network. [7M]

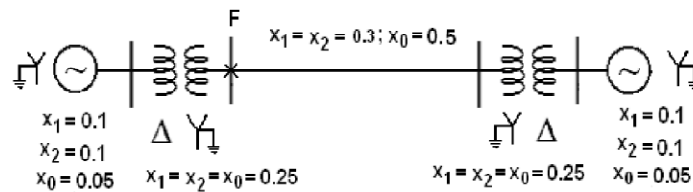5. A 3 phase transmission line operated at 33kV having resistance of  $5\Omega$  [14M]  
and reactance of  $20\Omega$  is connected to a generating station through  
15MVA step up transformer with 5% reactance. Two alternators are  
connected in parallel to the bus bar. First alternator is rated with  
10MVA, 11KV and 10% reactance and second alternator with 5MVA,  
11KV and 7.5% reactance. Calculate short circuit MVA, short circuit  
current and fault current in rms, if a symmetrical fault occurred at:  
(i) the end of the transmission line;  
(ii) high voltage terminals of the transformer.
6. a) What are symmetrical components? Explain their necessity in the [4M]  
calculation of unsymmetrical phase vectors.  
b) For the system shown in below figure, find the short circuit current, [10M]  
short circuit MVA and fault current if a LL fault occurs at point F.



7. a) Define the following terms: [6M]  
i) Steady state stability limit  
ii) Dynamic state stability limit  
iii) Transient state stability limit.
- b) Derive the expression of swing equation. Show the stability of rotating [8M]  
machines with the help of swing curves.

\*\*\*\*\*