

**III B. Tech I Semester Regular Examinations, October/November - 2018****POWER ELECTRONICS**

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70

Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)2. Answer **ALL** the question in **Part-A**3. Answer any **FOUR** Questions from **Part-B**

~~~~~

**PART -A**

1. a) Draw the turn – OFF characteristics of SCR. [2M]
- b) Explain the effect of source inductance in fully controlled bridge rectifier with continuous conduction. [2M]
- c) Draw the circuit diagram of a 3-phase full wave uncontrolled rectifier. [2M]
- d) Explain duty cycle in step up chopper operation [3M]
- e) What is the principle of operation of Inverter? [3M]
- f) Compare turn off mechanism of TRIAC and Thyristor [2M]

**PART -B**

2. a) What is power MOSFET? What are the types of power MOSFET? Write the difference between general purpose MOSFET and power MOSFET? [7M]
- b) Describe the basic behavior of thyristor using a two- transistor model. [7M]
3. What is phase angle controlled technique? Explain the operation of single – phase angle controlled rectifier. Derive the expression for average dc output voltage. Draw the relevant waveforms. [14M]
4. A three –phase full converter is connected to a load resistance of  $5\ \Omega$  and it is supplied from a 220 V, 50 Hz ac supply, If the firing angle of thyristor is  $\alpha = 30^\circ$ , Draw the relevant waveforms and determine i) average output voltage, ii) average output current, iii) rms output voltage and iv) rms output current. [14M]
5. a) Explain the operating principle of dc chopper with a suitable diagram. Draw the voltage and current waveforms of chopper. Derive expressions for average output voltage and rms output voltage. [10M]
- b) Discuss the principle of operation of Buck-Boost converter. [4M]
6. a) Describe the V-I characteristics of TRIAC and modes of operation. [7M]
- b) A single –phase half –wave ac voltage controller is connected with a load of  $R = 5\ \Omega$  with an input voltage of 230 V, 50 Hz. If the firing angle of thyristor is  $45^\circ$ , determine i) RMS output voltage, ii) Power delivered to load [7M]
7. a) What are pulse width modulated inverters? What are the different PWM techniques used in inverter? [7M]
- b) With the help of a neat circuit diagram and waveforms, explain the operation of 3-phase bridge inverter with R load. [7M]

\*\*\*\*\*



### III B. Tech I Semester Regular Examinations, October/November - 2018

# POWER ELECTRONICS

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70

Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)

2. Answer **ALL** the question in **Part-A**

3. Answer any **FOUR** Questions from **Part-B**

**PART -A**

1. a) Explain the turn – ON and turn – OFF time of SCR. [2M]
- b) Draw the 1-phase fully controlled rectifier circuit with freewheeling diode. [2M]
- c) In the case of a 3-phase , half controlled rectifier feeding a purely resistive load, if two values of the firing angle  $\alpha$  are measured from the point of natural commutation are 20 and 40 degrees , then obtain the extinction angles measured from the origin. [2M]
- d) Draw the static V-I characteristics of TRIAC. [3M]
- e) List the advantages and disadvantages of Boost converter. [3M]
- f) Compare VSI and CSI. [2M]

**PART –B**

- |    |    |                                                                                                                                                                                                                                                                                                                                                         |       |
|----|----|---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|-------|
| 2. | a) | Draw the V-I characteristics of a power MOSFET and explain different operating regions.                                                                                                                                                                                                                                                                 | [7M]  |
|    | b) | Draw the V-I characteristics of SCR and explain it briefly?                                                                                                                                                                                                                                                                                             | [7M]  |
| 3. | a) | A single phase 220 V, 1 kW heater is connected to a half-wave controlled rectifier and fed from a 220 V, 50 Hz ac supply, Determine the power absorbed by the heater when the firing angle is i) $\alpha = 30^\circ$ and ii) $\alpha = 90^\circ$ .                                                                                                      | [10M] |
|    | b) | Write the advantage of freewheeling diode in single-phase half-wave controlled rectifier with $RL$ load.                                                                                                                                                                                                                                                | [4M]  |
| 4. |    | Draw the circuit diagram of three-phase, half-wave controlled rectifier with $R$ load and explain its operating principle with voltage and current waveforms. Determine the following parameters for $R$ load with firing angle $\alpha = 60^\circ$ :<br>i) dc output voltage ii) Average dc load current iii) rms output voltage iv) rms load current. | [14M] |
| 5. | a) | Explain the different control strategies in DC-DC circuits?                                                                                                                                                                                                                                                                                             | [7M]  |
|    | b) | Discuss the Principle of operation of forward and fly back converters in CCM.                                                                                                                                                                                                                                                                           | [7M]  |
| 6. | a) | Describe working of 3-Phase AC-AC regulators with $R$ load only and draw the relevant waveforms.                                                                                                                                                                                                                                                        | [7M]  |
|    | b) | A single phase full-wave ac voltage controller is connected with a load of $R = 10 \Omega$ , with an input voltage of 230 V, 50 Hz. When the firing angle of thyristors is $45^\circ$ , determine i) power output at load, ii) average value of thyristor current and iii) rms value of thyristor current.                                              | [7M]  |
| 7. | a) | What is pulse width modulation? List the various PWM techniques. How do these differ from each other?                                                                                                                                                                                                                                                   | [7M]  |
|    | b) | A single-phase PWM inverter is fed from a 220 V dc supply and it is connected to a $RL$ load with $R=10$ ohms and $L=10$ mH. Determine the total harmonic distortion in the load current. Assume width of each pulse is $\pi/2$ and the output frequency is 50 Hz.                                                                                      | [7M]  |

\* \* \* \* \*



**III B. Tech I Semester Regular Examinations, October/November - 2018****POWER ELECTRONICS**

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70

Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)2. Answer **ALL** the question in **Part-A**3. Answer any **FOUR** Questions from **Part-B****PART -A**

1. a) Compare Power MOSFET and IGBT. [2M]
- b) What would be the input power factor in a 1-phase rectifier if extinction angle control is used for improving power factor with angle  $\beta$  is  $50^\circ$  [2M]
- c) A 3-phase controlled rectifier feeds a purely resistive load. The data are  $V_s = 220V$  (rms) and  $R_{ld} = 15$  ohms. If the firing angle  $\alpha$  is  $45^\circ$  then what would be the duration of conduction of thyristor. [2M]
- d) Discuss the time ratio control in a dc chopper [3M]
- e) Draw the waveforms for 1-phase fully controlled ac regulator with inductive load. [3M]
- f) Why a PWM inverter is superior to a square wave Inverter? [2M]

**PART -B**

2. a) Draw the switching characteristics of power MOSFETs. Define turn- ON delay time, rise time, turn – ON time, turn- OFF delay time, fall time and turn- OFF time. [7M]
- b) What are the different turning – ON methods of a thyristor? Explain each method. [7M]
3. a) Draw the circuit diagram of a single – phase full wave controlled rectifier using centre tap transformer with R load and find dc output voltage. [7M]
- b) A single phase fully controlled bridge converter with RL load is supplied from 220 V, 50 Hz ac supply. If the firing angle is  $45^\circ$ , determine i) average output voltage, ii) output current iii) input power factor. [7M]
4. a) Draw the circuit diagram of a three phase bridge converter with RL load. Discuss its working principle. Draw the voltage and current waveforms. Determine the following parameters: [14M]
  - i) dc output voltage
  - ii) average dc load current
  - iii) rms output voltage
  - iv) rms load current .
5. With the help of a neat circuit diagram and associated waveforms, discuss the operation of Buck-Boost converter. [14M]
6. a) Draw the single – phase bidirectional ac voltage controller with R load and explain its working principle with waveforms. [7M]
- b) Draw the waveforms for 3-phase a.c voltage regulator for R load for firing angle  $60^\circ$  [7M]
7. Explain the working of TRIAC as voltage controller with R load and draw the relevant waveforms. [14M]

\*\*\*\*\*

|'|'|'|'|'|'|'|'|'|'|'

### III B. Tech I Semester Regular Examinations, October/November - 2018

# POWER ELECTRONICS

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70

Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)

2. Answer **ALL** the question in **Part-A**

3. Answer any **FOUR** Questions from **Part-B**

**PART -A**

1. a) What is Sunbber circuit? [2M]
- b) In a 1-phase bridge type of controlled rectifier supplying RL load, under what conditions discontinuous conduction occurs. [2M]
- c) Draw a 3-phase half wave controlled converter circuit diagram and output voltage wave form for R load. [2M]
- d) List the advantages and disadvantages of Buck-Boost converter [3M]
- e) How shoot through fault will be prevented in VSI. [3M]
- f) What is meant by integrated cycle control [2M]

**PART –B**

- |    |    |                                                                                                                                                                                                                                                                                                                                                                            |        |
|----|----|----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|--------|
| 2. | a) | What is IGBT? What are the advantages of IGBT over power BJT and power MOSFET?                                                                                                                                                                                                                                                                                             | [7M]   |
|    | b) | Draw the V-I characteristics of a thyristor and explain different operating regions. What is the effect of Gate current on the V-I characteristics of a thyristor?                                                                                                                                                                                                         | [7M]   |
| 3. | a) | What is the effect of source inductance in single –phase full – wave controlled bridge rectifier with $RL$ load? (b) Draw the voltage and current waveforms                                                                                                                                                                                                                | [10 M] |
|    | b) | Explain how a free – wheeling diode improves power factor in a converter.                                                                                                                                                                                                                                                                                                  | [4M]   |
| 4. |    | Draw the circuit diagram of 3 – phase half –wave controlled rectifier with $RL$ load and explain its operating principle with voltage and current waveforms. Determine the following parameters for $RL$ load with firing angle $\alpha = 30^\circ$ :<br>i) dc output voltage ii) Average dc load current iii) rms output voltage<br>iv) rms load current v) Ripple factor | [14M]  |
| 5. |    | With help of neat circuit diagram and associated waveforms discuss the operation of a Buck converter in continuous conduction mode and discontinuous conduction mode.                                                                                                                                                                                                      | [14M]  |
| 6. |    | Derive the expression for rms output voltage of bidirectional 1-phase ac voltage controller with $RL$ load. And draw the relevant waveforms.                                                                                                                                                                                                                               | [14M]  |
| 7. |    | Explain the working of a 1-phase full bridge Inverter with $RL$ load. Draw the relevant output waveforms.                                                                                                                                                                                                                                                                  | [14M]  |

\*\*\*\*\*

