

III B. Tech I Semester Supplementary Examinations, December -2023
ELECTRICAL MEASUREMENTS AND INSTRUMENTATION

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70

Answer any **FIVE** Questions **ONE** Question from **Each unit**

All Questions Carry Equal Marks

UNIT-I

1. a) Explain the construction and working principle of PMMC Instrument. [8M]
 b) What are the advantages and disadvantages of M.I instruments? [6M]
 (OR)
2. a) Draw the equivalent circuit and phasor diagram of a current transformer. [9M]
 Derive an expression for ratio error.
 b) Compare C.T with P.T in any four aspects. [5M]

UNIT-II

3. a) Explain the construction and working principle of single phase Electro-dynamometer type Wattmeter with a neat diagram [9M]
 b) State the differences between LPF and UPF wattmeters. [5M]
 (OR)
4. a) Draw the circuit diagram of a basic slide wire D.C. potentiometer. Explain its working? [8M]
 b) Explain with the help of suitable diagram, how a D.C. potentiometer can be used for determination of an unknown resistance [6M]

UNIT-III

5. a) Draw the circuit diagram of a Wheatstone bridge and derive the conditions of balance. [7M]
 b) Draw the circuit diagram of Wien's bridge. Explain its working. [7M]
 (OR)
6. a) Draw the circuit diagram of Maxwell's bridge and phasor diagram under balance conditions. Derive the equations under balance conditions. [7M]
 b) How can unknown capacitance be measured using Desauty Bridge? [7M]

UNIT-IV

7. a) Give the classification transducers. [6M]
 b) Explain the working of Thermistors. State their applications. [8M]
 (OR)
8. a) Explain the working of photo diodes. [7M]
 b) Explain the principle of operation of Piezo electric transducers. [7M]

UNIT-V

9. a) Explain the working of digital energy meter with a diagram. [7M]
 b) How do you use digital multimeter to measure resistance? [7M]
 (OR)
10. Explain the working of CRO with neat block diagram. Explain the function of each block. Also, state its applications. [14M]

