

**II B. Tech II Semester Supplementary Examinations, November - 2018****SWITCHING THEORY AND LOGIC DESIGN**

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70

Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)2. Answer **ALL** the question in **Part-A**3. Answer any **FOUR** Questions from **Part-B**

~~~~~

**PART -A**


1. a) Write first 20 numbers in base-6 system? (3M)
- b) What is duality? (2M)
- c) Define combinational circuit? (2M)
- d) What is PAL? (2M)
- e) List out the application of counters? (3M)
- f) What is Mealy model? (2M)

**PART -B**

2. a) convert the following decimal numbers to the indicated base: (7M)
  - i) 7562.45 to Octal
  - ii) 1938.257 to hexadecimal
  - iii) 175.175 to binary
- b) Construct Hamming code for BCD 0110. Use even parity. (7M)
3. a) Minimization of function f using K-map (7M)
 
$$f(A,B,C,D) = \sum(0,2,3,4,6,7,8,10) + d(12,13,14,15)$$
- b) Minimize the given 5 variable function using QM Tabular Method (7M)
 
$$f = \sum (2, 4, 9, 10, 11, 12, 19, 20, 21, 22, 23, 24, 25, 26, 29, 31).$$
4. a) Draw and explain about BCD adder circuit Excess3 adder circuit (7M)
- b) Explain in detail about 4-bit digital comparator (7M)
5. a) Implement  $f(A,B,C,D) = \sum(0,1,3,5,6,8,9,11,12,13)$  using PROM and explain its procedure (7M)
- b) Design and implement Full adder with PLA (7M)
6. a) With the aid of external logic, convert D type flip-flop to a T flip-flop (7M)
- b) Explain about decade ripple counter (7M)

7. a) For the state diagram shown in below fig, design using J-K Flip-flop

(7M)

 

- b) Design a sequence detector circuit to detect a serial input sequence of 1010. it should produce an output 1 when the input pattern has been detected.

(7M)