

Code No:R164202B

R16

Set No. 1

IV B.Tech II Semester Regular Examinations, September - 2020
FLEXIBLE ALTERNATING CURRENT TRANSMISSION SYSTEMS
(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70

Question paper consists of Part-A and Part-B

Answer ALL sub questions from Part-A

Answer any FOUR questions from Part-B

PART-A(14 Marks)

1. a) List out the importance of controllable parameters. [3]
- b) What are the principal types of current sourced converters? [2]
- c) How do you improve the transient stability using shunt compensation? [3]
- d) What are the methods of controlling the reactive power? [2]
- e) What are the various types of variable impedance type series compensators? [2]
- f) Why you need UPFC. [2]

PART-B(4x14 = 56 Marks)

2. a) Explain the dynamic stability considerations of a transmission interconnections. [7]
- b) Describe the possible benefits from FACTS technology. [7]
3. a) Discuss the basic concept of voltage source converter. [7]
- b) Explain the operation of three phase bridge converter with diagrams. [7]
4. Explain the mid-point voltage regulation for line segmentation with necessary diagrams and expressions. [14]
5. a) Explain the regulation slope of static VAr generator with block diagram. [7]
- b) Describe the VAr reserve control of static compensator. [7]
6. a) Discuss the concept of series capacitive compensation with necessary expressions. [7]
- b) What is the summary of functional requirements of series compensation? [7]
7. Explain the basic operating principle of UPFC with diagrams. [14]



Code No:R164202B

R16

Set No. 2

IV B.Tech II Semester Regular Examinations, September - 2020

FLEXIBLE ALTERNATING CURRENT TRANSMISSION SYSTEMS

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70

Question paper consists of Part-A and Part-B

Answer ALL sub questions from Part-A

Answer any FOUR questions from Part-B

PART-A(14 Marks)

1. a) What are the basic types of FACTS controllers? [2]
- b) What is the basic concept of voltage source converter? [3]
- c) What is the need of line voltage support to prevent voltage instability? [3]
- d) What is meant by thyristor switched capacitor? [2]
- e) What is meant by thyristor controlled series capacitor? [2]
- f) What is meant by UPFC? Draw its diagram. [2]

PART-B(4x14 = 56 Marks)

2. a) What limits loading capability in AC power transmission system. Discuss them. [7]
- b) Explain the losses and speed of switching of high power devices. [7]
3. a) Discuss the operation of single phase full wave bridge converter. [7]
- b) Derive the expressions for fundamental and harmonic voltages for a three phase bridge converter. [7]
4. Describe the improvement of transient stability using shunt compensation with necessary diagrams. [14]
5. a) Compare the different types of static VAR generators. [7]
- b) Derive the transfer function of SVC and STATCOM. [7]
6. Describe the thyristor switched series capacitor with neat diagrams and expressions. [14]
7. Explain the conventional transmission control capabilities of UPFC with diagrams and expressions. [14]

Code No:R164202B

R16

Set No. 3

IV B.Tech II Semester Regular Examinations, September - 2020
FLEXIBLE ALTERNATING CURRENT TRANSMISSION SYSTEMS
(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70

Question paper consists of Part-A and Part-B

Answer ALL sub questions from Part-A

Answer any FOUR questions from Part-B

PART-A(14 Marks)

1. a) What are the benefits from FACTS controllers? [3]
- b) What are the basic categories of self-commutating converters? [2]
- c) What are the objectives of shunt compensation? [3]
- d) What are the functions provided by the control scheme of TSC-TCR type VAr generator? [2]
- e) What is meant by thyristor switched series capacitor? Draw its diagram. [2]
- f) What is the need of UPFC? [2]

PART-B(4x14 = 56 Marks)

2. a) What are the opportunities of FACTS? How they are fulfilled in AC power transmission? [7]
- b) What are the basic types of FACTS controllers? Discuss them with neat diagrams. [7]
3. a) How do you determine dominant harmonics in the square wave output voltage of a single phase inverter? [7]
- b) What are the merits and demerits of current source versus voltage source converters? [7]
4. a) Explain the power oscillation damping with shunt compensation. [7]
- b) What is the summary of shunt compensator requirements? [7]
5. Describe the TSC-TCR type VAr generator with necessary diagrams. [14]
6. a) Explain the improvement of transient stability using static series compensator. [7]
- b) Briefly discuss the GTO thyristors controlled series capacitor. [7]
7. Explain the independent real and reactive power flow control of UPFC with diagrams. [14]

Code No:R164202B

R16

Set No. 4

IV B.Tech II Semester Regular Examinations, September - 2020
FLEXIBLE ALTERNATING CURRENT TRANSMISSION SYSTEMS
(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70

Question paper consists of Part-A and Part-B

Answer ALL sub questions from Part-A

Answer any FOUR questions from Part-B

PART-A(14 Marks)

1. a) What are the various types of high power thyristor devices? [2]
- b) What is the primary difference between current source converter and voltage source converter? [3]
- c) What is the need of mid-point voltage regulation for line segmentation? [3]
- d) What is meant by STATCOM? Draw its diagram. [2]
- e) What are the objectives of series compensation? [2]
- f) Draw the circuit diagram of UPFC. [2]

PART-B(4x14 = 56 Marks)

2. a) Why we need transmission interconnections? [5]
- b) Illustrate the power flow in an AC System. [9]
3. a) Derive the expression for square wave voltage harmonics for single phase bridge. [7]
- b) Explain the operation of threephase current source converter. [7]
4. a) What are the objectives of shunt compensation? [5]
- b) Explain how you prevent voltage instability using end of line voltage support. [9]
5. a) Describe the thyristor switched capacitor with neat diagrams. [9]
- b) Compare SVC and STATCOM type of VAR generators. [5]
6. Describe the thyristor controlled series capacitor with neat diagrams and expressions. [14]
7. Compare the UPFC to controlled series compensators with necessary diagrams [14]