

II B. Tech II Semester Supplementary Examinations, November - 2019
PULSE AND DIGITAL CIRCUITS
 (Com to ECE, EIE, ECC)

Time: 3 hours

Max. Marks: 70

Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)

2. Answer **ALL** the question in **Part-A**

3. Answer any **FOUR** Questions from **Part-B**

~~~~~

**PART -A**

- |       |                                                                                                                            |    |
|-------|----------------------------------------------------------------------------------------------------------------------------|----|
| 1. a) | Define attenuator?                                                                                                         | 2M |
| b)    | Draw the transfer characteristics of a diode clipper and define transmitting Region, limiting region, and clipping region? | 2M |
| c)    | Define $t_{on}$ and $t_{off}$ of a transistor.                                                                             | 2M |
| d)    | Calculate the gatewidth of a monostable multivibrator $R=10k\Omega$ and $c=10\mu F$ ?                                      | 3M |
| e)    | Draw the sweep voltage and sawtooth waveforms and name the parts in that Waveform?                                         | 2M |
| f)    | Define positive and negative logic and give the examples?                                                                  | 3M |

**PART -B**

- |       |                                                                                                                                                                       |    |
|-------|-----------------------------------------------------------------------------------------------------------------------------------------------------------------------|----|
| 2. a) | Calculate the lowest square wave frequency that can be passed by an amplifier With a lower 3-db frequency of 5 Hz. If the maximum allowable tilt in the Output is 2%. | 7M |
| b)    | Explain about RLC ringing circuit?                                                                                                                                    | 7M |
| 3. a) | Draw the circuit diagram of an emitter –coupled clipping circuit and draw its Transfer characteristics indicating all intercepts, slopes and voltage levels.          | 7M |
| b)    | Design a diode clamper to restore a d.c level of +3 volts to an input signal Of peak to peak value of 10 volts. Assume drop across diode is 0.6 volts.                | 7M |
| 4. a) | Explain how transistor acts as switch. Draw base and collector waveforms and indicate all the time intervals.                                                         | 7M |
| b)    | Explain applications of Schmitt trigger.                                                                                                                              | 7M |
| 5. a) | Explain the need of trigger circuit in monostable multivibrator? List out types of trigger circuits?                                                                  | 7M |
| b)    | Explain about free running multivibrator.                                                                                                                             | 7M |
| 6. a) | Explain how UJT is used for sweep circuit.                                                                                                                            | 7M |
| b)    | Draw the circuit of a two stage transistor bootstrap circuit to get an exactly linear Sweep.                                                                          | 7M |
| 7. a) | How pedestal can be reduced in sampling gate? List the applications of Sampling gates.                                                                                | 7M |
| b)    | Draw and explain the basic CMOS inverter circuit.                                                                                                                     | 7M |