

III B. Tech I Semester Supplementary Examinations, October/November -2018**LINEAR & DIGITAL IC APPLICATIONS**

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70

- Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)
 2. Answering the question in **Part-A** is compulsory
 3. Answer any **THREE** Questions from **Part-B**

PART -A

- 1 a) Explain the significance of level translator [3M]
- b) Define CMRR and PSRR. [3M]
- c) What is an instrumentation amplifier? [4M]
- d) Draw the block diagram of a PLL? [4M]
- e) What are the advantages of active filters over passive filters? [4M]
- f) Define the terms Conversion time, Percentage resolution related to ADC. [4M]

PART -B

- 2 a) Draw the circuit diagram of a basic differential amplifier and explain its transfer characteristics. [8M]
- b) Draw the circuit diagram of dual input unbalanced output differential amplifier and derive the expression for dc analysis. [8M]
- 3 a) Discuss briefly about the DC characteristics of an operational amplifier? [8M]
- b) Define the terms: SVRR, Input bias current, Input offset voltage, Gain bandwidth product. [8M]
- 4 a) With a neat sketch explain the principle of operation of Antilog amplifier. [8M]
- b) Design a differentiator to differentiate an input signal that varies in frequency from 100Hz to 10 KHz. If a sine wave of 1.2V Peak at 10 KHz is applied to the differentiator of part, draw its output wave form. [8M]
- 5 a) Why the name was given to 555 Timer. Draw monostable multivibrator using 555 Timer and explain the operation. [8M]
- b) Design an Astable multivibrator having an output frequency 15 KHz with duty cycle of 40%. [8M]
- 6 a) With neat circuit diagram explain the operation of 2nd order butter worth HPF and derive an expression for voltage gain. [8M]
- b) Design a Band Pass filter with $f_c = 1$ KHz, $Q = 3$ and $A_f = 10$. Draw the circuit with all the components. [8M]
- 7 a) Draw the schematic circuit diagram of dual-slope A/D converter and explain its operation. Derive expression for output voltage. [8M]
- b) Define important performance specifications of Digital to Analog converters and list their typical values. [8M]
